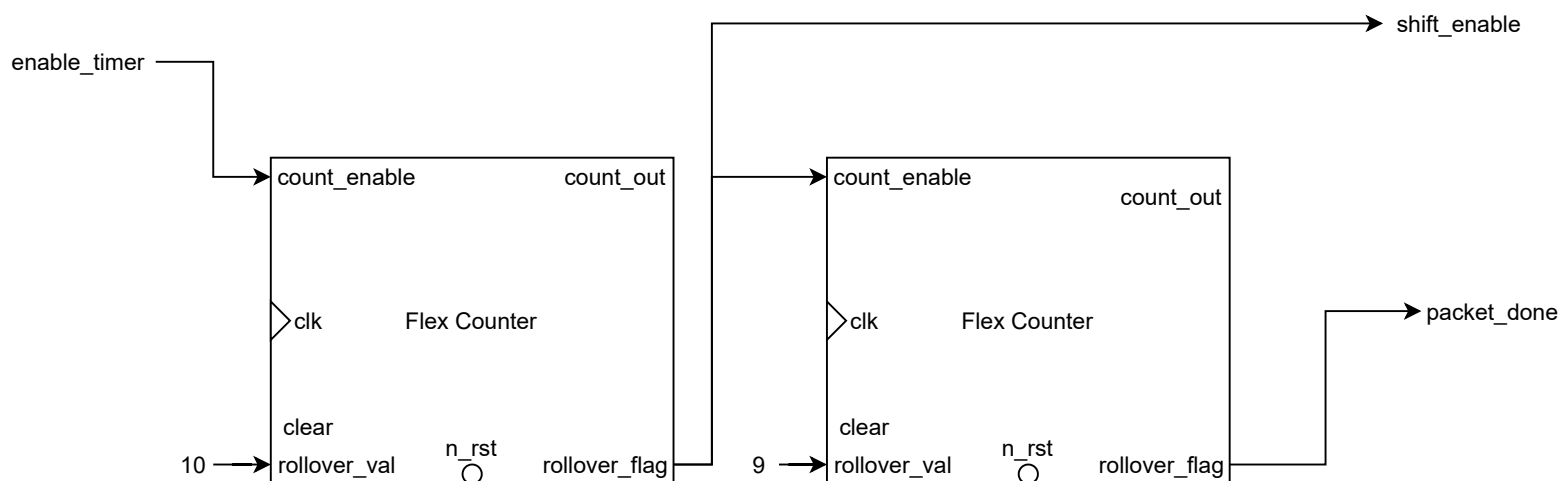


enable_timer: connected to count_enable of first timer
shift_enable: connected to rollover flag of first timer
packet_done: connected to rollover flag of second timer



First counter counts to 10 starting when enable_timer is asserted. When it reaches 10, it outputs a strobe for shifting in a new value into the 9-bit register and to count another bit shifted in the second counter.

Second counter counts the bits based on the rollover flag from the first counter, then outputs packet_done using its rollover flag when it reaches 9 bits counted.